

2572**Code : 15EC-11T**Register
Number

--	--	--	--	--	--	--	--

I Semester Diploma Examination, Nov./Dec. 2015**BASIC OF ELECTRICAL & ELECTRONICS
ENGINEERING****Time : 3 Hours |****[Max. Marks : 100]**

- Note :** (i) Answer any **six** questions from Part-A.
(ii) Answer any **seven** full questions from Part-B.

PART – A

1. Define power and energy along with their units.

BETA CONSOLE!**5**

2. State and explain Kirchoff's current law.

Diploma - [All Branches]

Beta Console Education

5

3. Define charge and field strength.

5

4. State Lenz's law.

Diploma Question Papers [2015-19]

Beta Console Education

5

5. Define r.m.s. and average value of AC signal and write their equations.

5

6. Describe AC behaviour in pure capacitive circuit.

5

7. Describe step-up and step-down transformers.

5

8. List and explain specifications of resistors.


5

9. Classify capacitors based on dielectric materials used and write one application each. **5**

[Turn over

PART - B

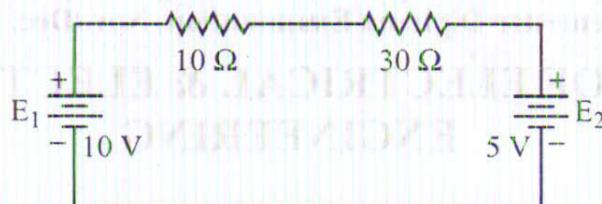10. (a) Develop an expression for total resistance of three resistances connected in parallel. 5
 (b) Compute current through the resistor $10\ \Omega$ in the following circuit. 5



11. Explain constructional features of lead-acid battery. 10
 12. Discuss series and parallel combination of capacitors. 10
 13. (a) State and explain Faraday's second law of electro-magnetic induction. 6
 (b) Define inductive reactance and quality factor. 4

BETA CONSOLE!

14. (a) Analyze AC behaviour in RC circuit. 6
 (b) A circuit consist of resistance of $10\ \Omega$, inductance of $0.2\ H$ [Diploma Question Papers All Branches] and capacitance of $10\ \mu F$ with a $50\ Hz$ supply AC source. Compute impedance. 4

15. A resistance of $20\ \Omega$ and an inductance of $10\ H$ are connected in series to an AC supply of $100\ V$, $50\ Hz$. Compute : 10
 (i) impedance
 (ii) current
 (iii) power factor



Diploma Question Papers [2015-19]

Beta Console Education

16. (a) Describe working principle of auto transformer. 5
 (b) Calculate EMF induced in the secondary of transformer of 100 turns, when the primary is operating on $50\ Hz$ supply produces a maximum flux of 0.04 webers. 5

17. (a) Describe operation of DC motors. 7
 (b) List applications of pulse transformer. 3

18. (a) Explain principle of operation of VDR. 6
 (b) List specifications of inductors. 4

19. (a) Describe principle of operation of linear thermistor. 6
 (b) List features of linear potentiometer. 4